

Reliability and Quality of Distribution System

The Part of Power System which distributes electric power for local use is known as distribution system

~~Power~~ ^{Fig 5.1}

Distribution

I) Primary AC Distribution.

- (i) Radial Feeder -
- (ii) Parallel Feeder. Dec-14
Jun-14
- (iv) Loop Feeder -
- (iv) Interconnected N/w system.

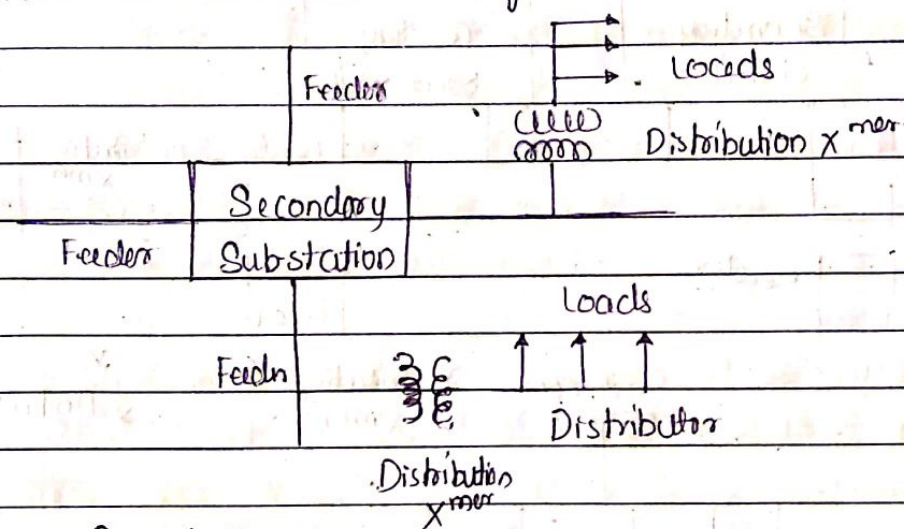


Fig 5.1 Radial Feeder S/m

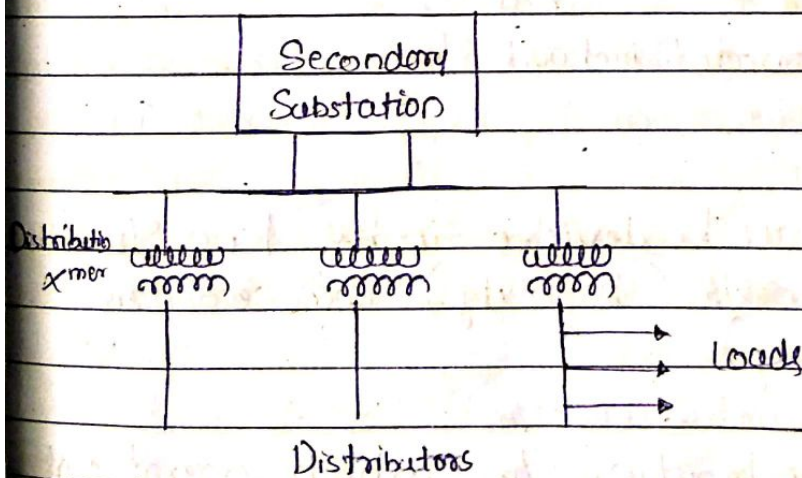


Fig 5.2 Parallel Feeder S/m

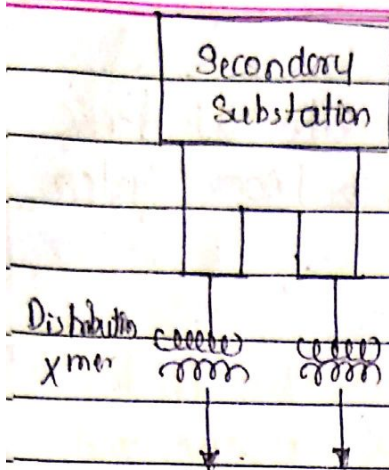


fig 5.3 loop Feeder s/m

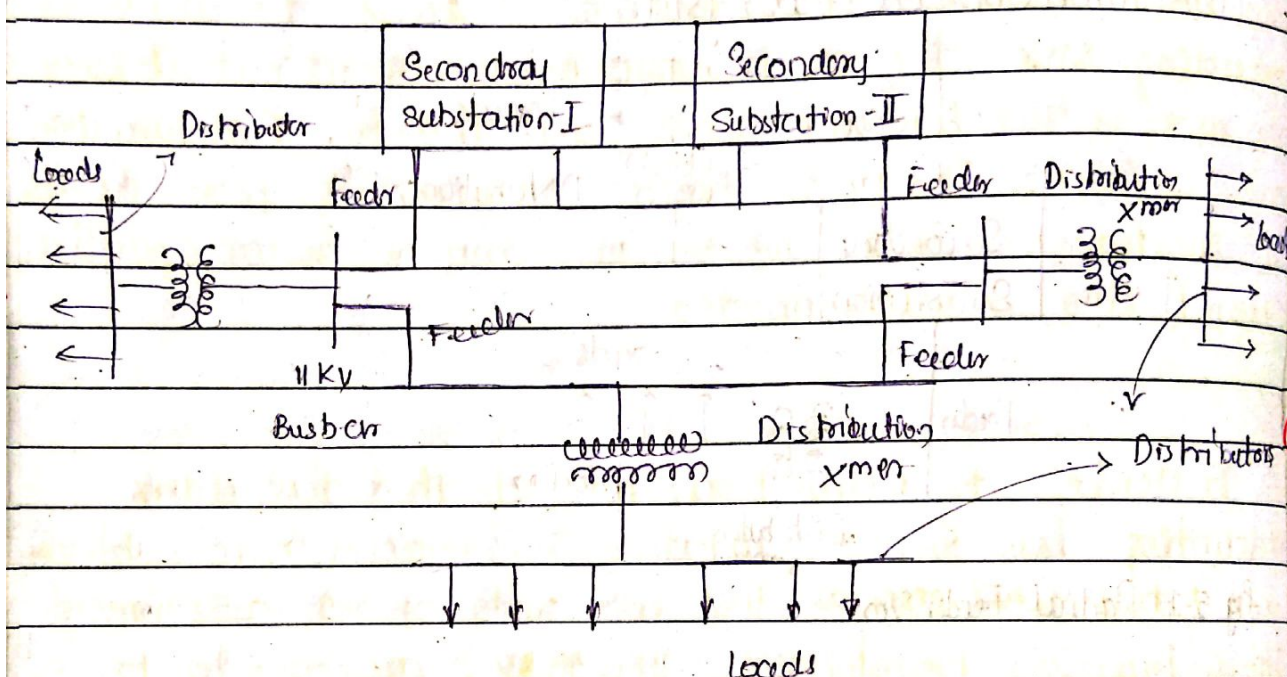


fig - 5.4 Inter connected Network s/m

Introduction

Distribution s/m may be divided in two s/m known as primary distribution s/m (High vltg) and secondary distribution s/m (Low vltg)

1) Primary AC Distribution s/m

It is part of AC distribution s/m which operates at voltages such as (3.3 kV, 6.6 kV, 11 kV or higher even) some what higher than that of general utility (440/220 or 440/230) and handled large blocks of power. The primary distribution is universally carried out by 3-phase, 3wire s/m

Electric power from Generating station is transmitted through extra high tension T.L.s vltgs 33kV to 440 kV to various substations near to the located cities at the 1st substation.

The vltg. is stepped down to 11kV, 6.6kV or 33kV with help of power transformers for primary distribution.

The 33/11kV 2nd substations are usually located in the area having load requirement of the order 5 MVA and normally a primary distribution line or a feeder is desired to carry a load of 1-2 MVA so the no. of feeders originating from the 2nd substation of 33/11kV is 3-4 MVA for the load exceeding MVA. The 2nd transmission is carried out at 66kV so as to reduce the line losses and therefore 2nd substations are 66/11kV. The no. of feeders originating from the 66/11kV 2nd substation is 6-8. The feeders may be radial, parallel, loop (ring) or interconnected.

1) Radial Feeders

It derives its name from the fact that the feeders radiate from the 2nd substation and branches in to subfeeders and laterals which extends in to all parts of area subconnected. The distribution transformers (11kV/440V) are connected to primary feeder, subfeeders and laterals, usually through fuse cutouts. Radial feeder is simplest and most economical & most commonly used one. It is advantageous for supply power to industrial load near the 2nd SS, Isolated loads such as tube wells, and areas of low load density such as villages.

24/4/11

Imp

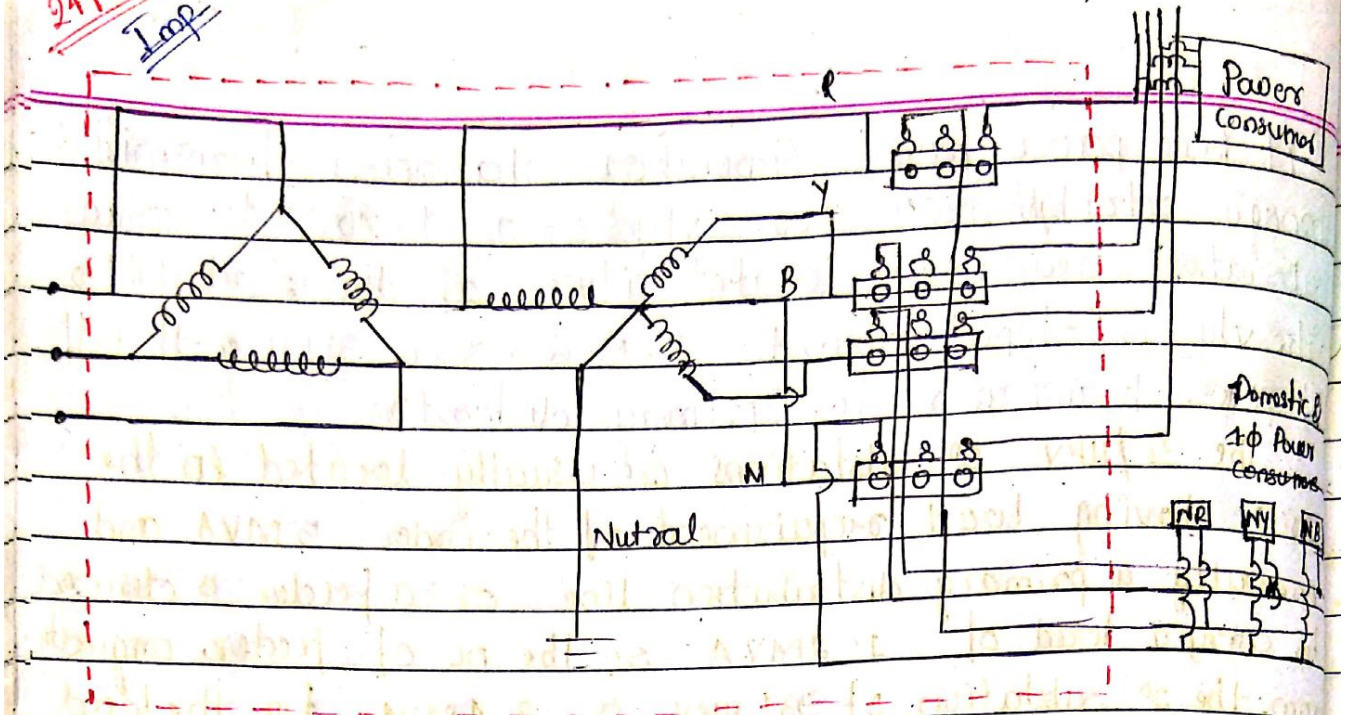


fig - 5.5 3- ϕ 4wire Distribution s/m

Consequences of Disconnecting neutral in a 3 ϕ 4wire s/m

AC Distribution Calculation

AC Distribution calculation differs from DC distribution in the following aspects

- I) In case of DC s/m the v/tg drop is due to resistance alone. However in AC s/m the v/tg drops are due to combined effect RLC.
- II) In DC s/m additions and subtractions of c/r or voltages are done arithmetically but in case of AC s/m these operations are done vectorially.
- III) In AC s/m power factor has to be taken into account. Loads tapped off from the distribution are generally at different power factors.

There are two ways of referring power factor.

a) It may be referred to supply or receiving end v/tg which is regarded as reference vector.

b) It is referred to the load point itself.

There are several ways of solving AC distribution s/m.

However symbolic notation method has been found to be most convenient for this purpose. In this method v/tg, c/r's

and impedances are expressed in complex notation & the calculations made exactly like in the DC distribution M.

Methods of Solving AC Distribution Problems

In AC distribution calculation p.f. of various load c/nts have to be considered. Since currents in diff sections of the distributor will be the vector sum of load currents and not an arithmetic sum.

The P.f. of the load may be given


- 1) With respect receiving end or sending end v/tg
- 2) w.r.t load v/tg itself

Imp ^{Case} * Power factor referred to receiving end v/tg

Consider an AC distributor AB with concentrated loads of I_1 and I_2 tapped off at points C and B as shown in below fig - 5.6

Taking the receiving end voltage V_B as the reference vector, let lagging p.f.'s at C and B be $\cos\phi_1$ and $\cos\phi_2$ w.r.t V_B

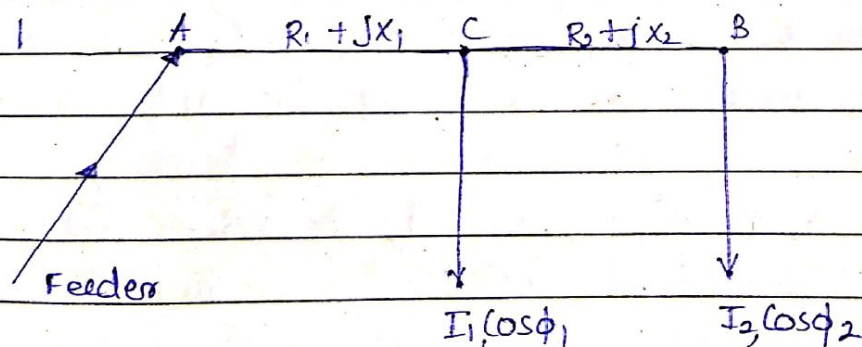Let R_1, X_1 and R_2, X_2 be the resistance & reactance of sections 'AC' and 'CB' of the distributor



Impedance of section AC is

$$\vec{Z}_{AC} = R_1 + jX_1 \quad \text{--- (5.1)}$$

Impedance of section CB is

$$\vec{Z}_{CB} = R_2 + jX_2 \quad \text{--- (5.2)}$$

Load current at point C

$$\vec{I}_1 = I_1 (\cos\phi_1 - j \sin\phi_1) \quad \text{--- (5.3)}$$

Load current at point B

$$\vec{I}_2 = I_2 (\cos\phi_2 - j\sin\phi_2) \quad (5.4)$$

Current in section CB

$$\vec{I}_{CB} = \vec{I}_2 = I_2 (\cos\phi_2 - j\sin\phi_2) \quad (5.5)$$

Current in section AC

$$\vec{I}_{AC} = \vec{I}_1 + \vec{I}_2$$

$$\vec{I}_{AC} = I_1 (\cos\phi_1 - j\sin\phi_1) + I_2 (\cos\phi_2 - j\sin\phi_2) \quad (5.6)$$

Voltage drop in section CB

$$\begin{aligned} \vec{V}_{CB} &= \vec{I}_{CB} \cdot \vec{Z}_{CB} \\ &= I_2 (\cos\phi_2 - j\sin\phi_2) (R_2 + jX_2) \quad (5.7) \end{aligned} \quad \left| \begin{array}{l} \therefore (5.5) \\ (5.2) \end{array} \right.$$

Voltage drop in section AC

$$\vec{V}_{AC} = \vec{I}_{AC} \cdot \vec{Z}_{AC}$$

From eqn 5.6 and 5.1

$$\therefore \vec{V}_{AC} = (\vec{I}_1 + \vec{I}_2) (R_1 + jX_1) \quad (5.8)$$

$$= [I_1 (\cos\phi_1 - j\sin\phi_1) + I_2 (\cos\phi_2 - j\sin\phi_2)] \cdot (R_1 + jX_1) \quad (5.9)$$


Sanisodical voltage

$$\vec{V}_A = \vec{V}_B + \vec{V}_{BC} + \vec{V}_{AC} \quad (5.10)$$

$$\vec{I}_A = \vec{I}_1 + \vec{I}_2$$

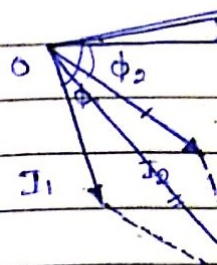(ii) Power factor

Suppose the power factor is $\cos\phi$ between V_B and $\vec{I}_2$ shown in fig



Voltage drop

$$\vec{I}_2 \vec{Z}_{CB}$$

Voltage

$$\vec{V}_C =$$

$$\vec{V}_C =$$

Now $\vec{I}_1$

also $\vec{I}_1$

$$\vec{I}_1$$

Now, $\vec{I}_A$

voltage

$$\vec{V}_{AC} =$$


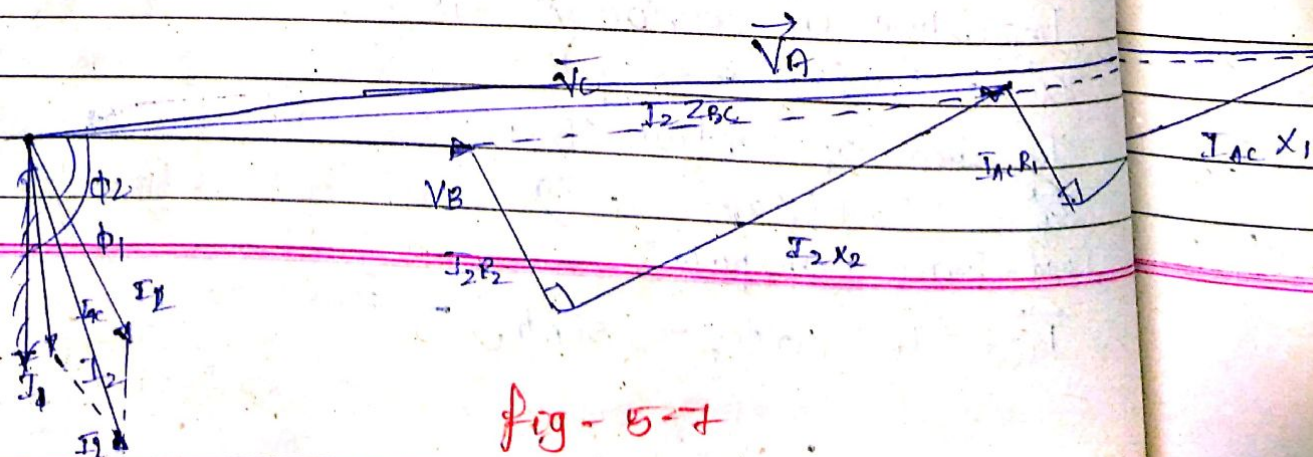


Fig-5-7

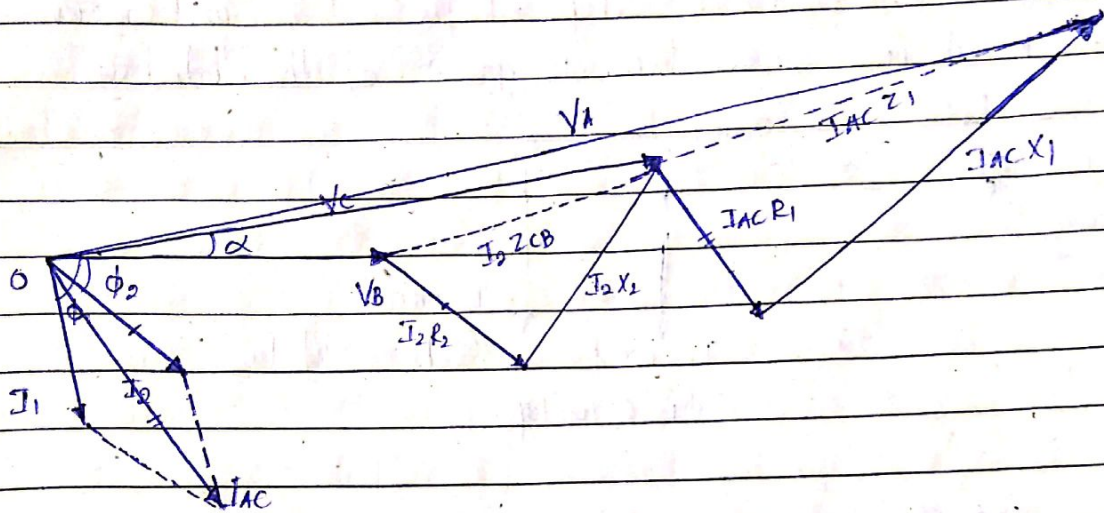(ii) Power factors referred to respective load voltages

Suppose the power factor of loads in the previous fig-5.7 are referred to their respective load voltages. ϕ_1 is the phase angle between V_C & I_1 and ϕ_2 is the phase angle between V_B & I_2 . The vector diagram under these conditions is shown in fig-5.8



Voltage drop in section CB

$$\vec{I}_2 \vec{Z}_{CB} = I_2 (\cos \phi_2 - j \sin \phi_2) (R_2 + jX_2)$$

Voltage at point C

$$\vec{V}_C = V_B + \text{drop in the section CB}$$

$$\vec{V}_C = V_C \angle \alpha \text{ (say)}$$

Now $\vec{I}_1 = I_1 \angle -\phi_1$ with respect to voltage V_C

also $I_1 = I_1 \angle -(\phi_1 - \alpha)$ wrt voltage V_B

$$\vec{I}_1 = I_1 (\cos(\phi_1 - \alpha) - j \sin(\phi_1 - \alpha))$$


$$\text{Now, } \vec{I}_{AC} = \vec{I}_1 + \vec{I}_2$$

Voltage drop in section AC

$$\vec{V}_{AC} = \vec{I}_{AC} \cdot \vec{Z}_{AC}$$

$$\therefore \text{Voltage at point A} = V_A$$
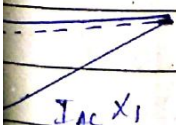
$$\text{i.e. } \vec{V}_A = \vec{V}_B + \text{drop in section CB} + \text{drop in section AC}$$




A 2 ϕ AC distributor AB 300m long is fed from end A and is loaded as under

I) 100 A at point 707 pf lagging, 200m from point A

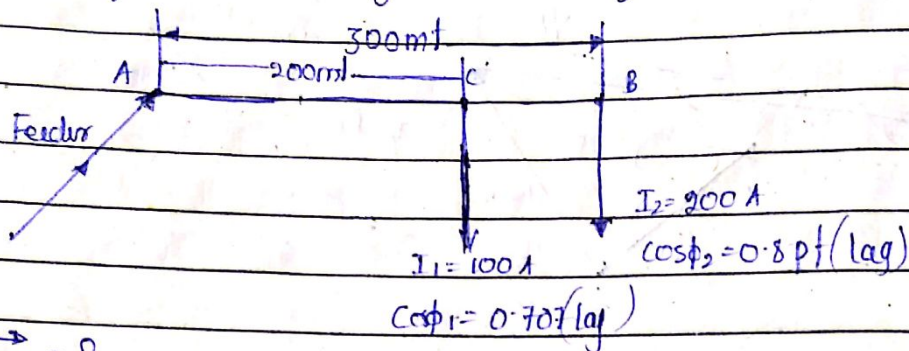II) 200 A at 0.8 pf 300m from point A.

The load resistance & reactance of the distributor is 0.2 Ω and 0.1 Ω / km calculate the total v_t drop in the distributor. The load pfs referred to the v_t at far end (not receiving end) ^{Case I}

below fig shows single line diagram of the distributor



$$\vec{V}_{AB} = ?$$

$$\vec{V}_{AB} = \vec{V}_{AC} + \vec{V}_{BC}$$

$$\vec{V}_{AB} = \vec{V}_{BC} + \vec{V}_{AC}$$

$$= \vec{I}_{BC} \vec{Z}_{CB} + \vec{I}_{AC} \vec{Z}_{AC}$$

$$\text{But } \vec{I}_{AC} = \vec{I}_1 + \vec{I}_2$$

$$\text{Now } \vec{I}_1 = I_1 (\cos \phi_1 + j \sin \phi_1)$$

$$\vec{I}_2 = I_2 (\cos \phi_2 - j \sin \phi_2)$$

also

$$\vec{Z}_{AC} = (0.2 + j0.1) \times \frac{200}{1000} = (0.04 + j0.02) \Omega$$

$$\vec{Z}_{CB} = (0.2 + j0.1) \times \frac{100}{1000} = (0.02 + j0.01) \Omega$$

Taking voltage at the far end V_B as the reference vector we have load c/n at point B

$$\text{i.e. } \vec{I}_2 = I_2 (\cos \phi_2 - j \sin \phi_2)$$

$$= 200 (0.8 - j0.6)$$

$$= (160 - j120) \text{ A}$$

$$I_2 = 200 \angle -36.86^\circ \text{ A}$$

load c/n at point C

$$\vec{I}_1 = I_1 (\cos \phi_1 - j \sin \phi_1)$$

$$= 100 (0.707 - j0.707)$$

$$\vec{I}_1 = (70.7 - j70.7) \text{ A}$$

$$I_1 = 99.98 \angle -45^\circ \text{ A}$$

$$\vec{I}_{CB} = \vec{I}_2 = 200 (160 - j120) \text{ A} = 200 \angle -36.86^\circ$$

Current in section AC

$$\vec{I}_{AC} = \vec{I}_1 + \vec{I}_2$$

$$= 200 \angle -36.86^\circ + 99.98 \angle -45^\circ$$

$$\vec{I}_{AC} = 230.71 - j190.66 \text{ A}$$

$$I_{AC} = 299.307 \angle -39.57^\circ \text{ A}$$

Voltage drop at section CB

$$\vec{V}_{CB} = \vec{I}_{CB} \cdot \vec{Z}_{CB}$$

$$= (200 \angle -36.86^\circ) (0.02 + j0.01)$$

$$\vec{V}_{CB} = (4.47 - j0.799) \text{ V}$$

$$\vec{V}_{CB} = 4.47 \angle -10.3^\circ$$

Voltage drop at section AC

$$\vec{V}_{AC} = \vec{I}_{AC} \cdot \vec{Z}_{AC}$$

$$= 299 \angle -39.57^\circ \times (0.04 + j0.02)$$

$$= 13.385 \angle -13.01^\circ$$

$$\vec{V}_{AB} = \vec{V}_{AC} + \vec{V}_{CB}$$

$$= (13.385 \angle -13.01^\circ) + (4.47 \angle -10.3^\circ)$$

$$= 17.85 \angle -12.33^\circ$$

$$\vec{V}_{AB} =$$

$$V_{AB} = 17.85$$